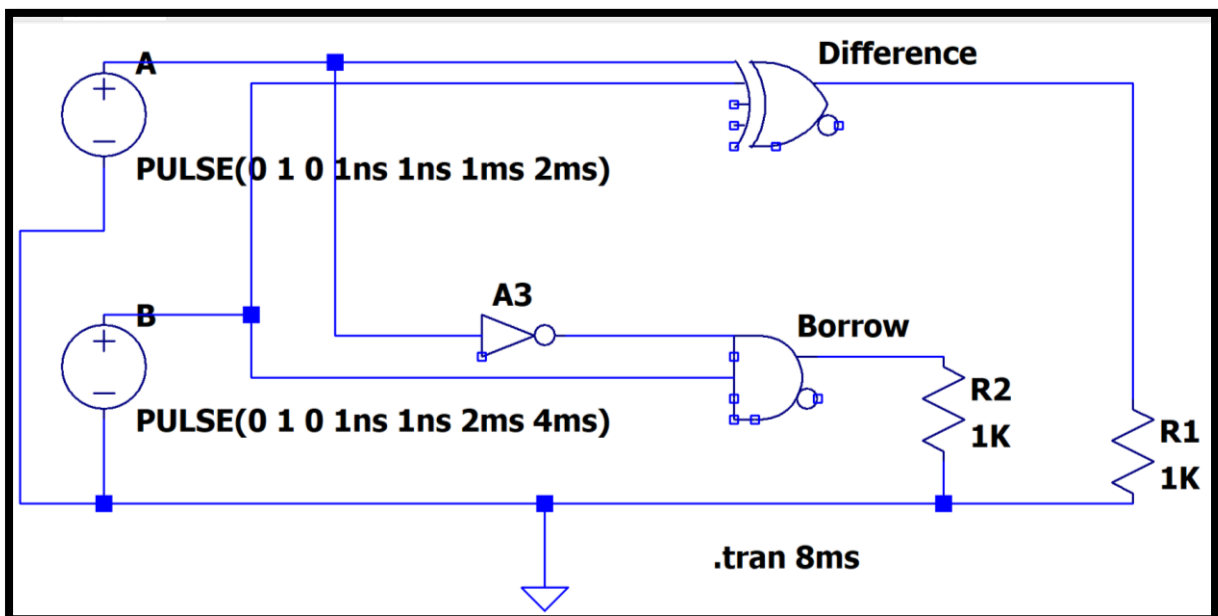

CSE1003 LAB-4

BY ASHUTOSH ARDU

REGISTRATION NUMBER -20BRS1262

HALF SUBTRACTOR

DIAGRAM:



OUTPUT:


The first one is A.

The second one is B.

The third one is Difference.


The fourth one is Borrow.



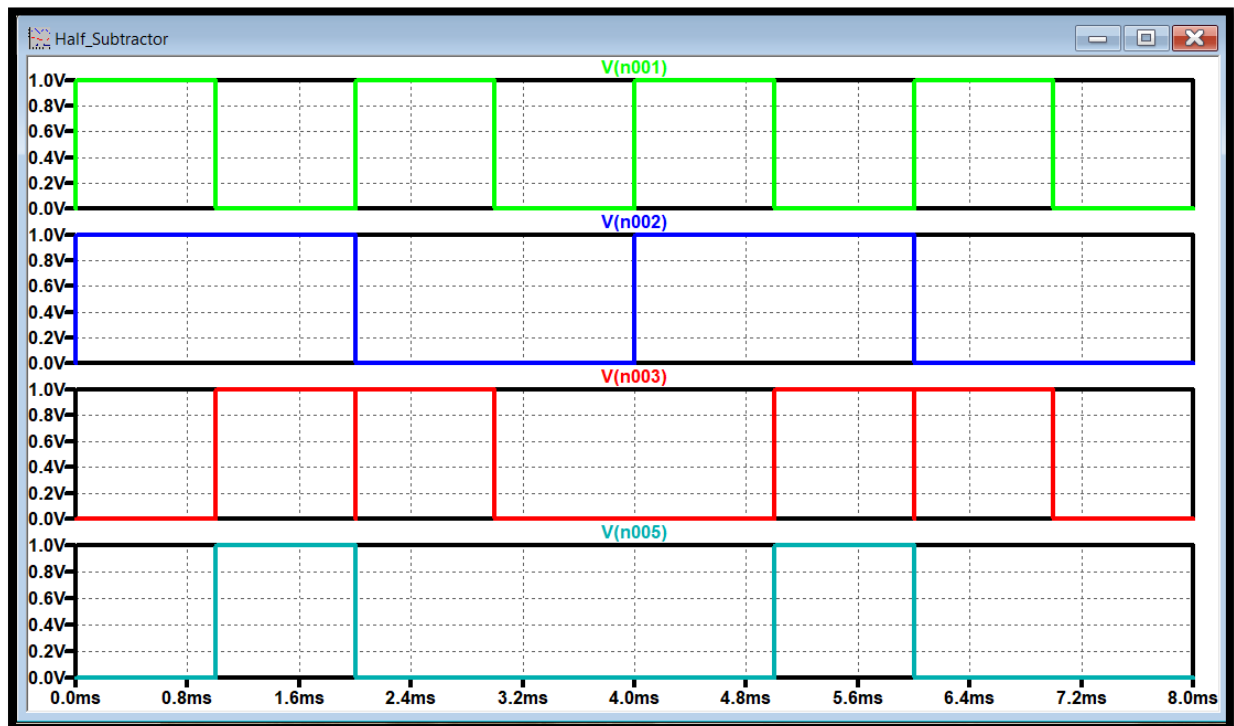

FULL SUBTRACTOR

DIAGRAM:

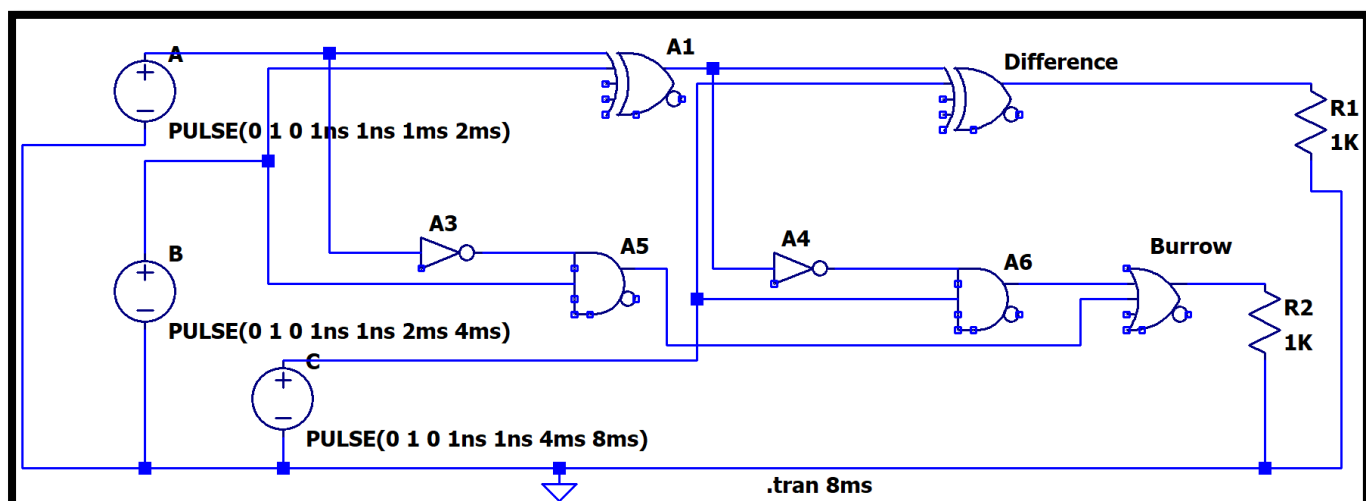

OUTPUT:



The first one is A.

The second one is B.

The third one is C.

The fourth one is Difference.

The fifth one is Borrow.

