


---

# *CSE1003-LAB*

---


## AND GATE

## DIAGRAM

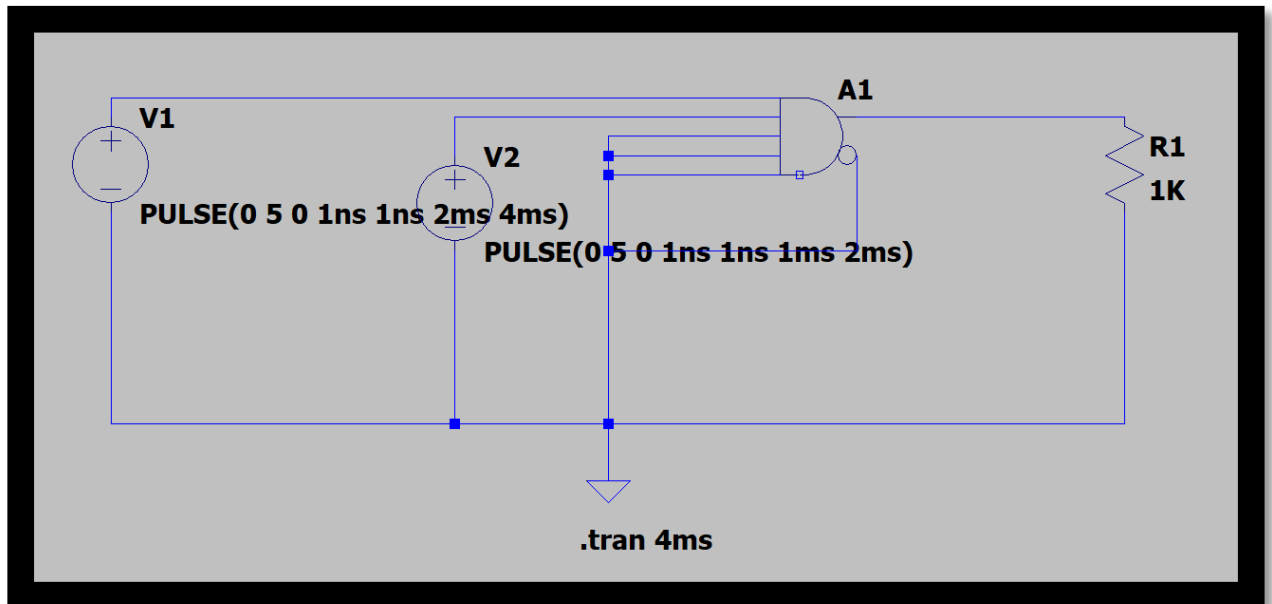


## OUTPUT



 


NOT GATE


DIAGRAM

 


## OUTPUT

 

# OR GATE

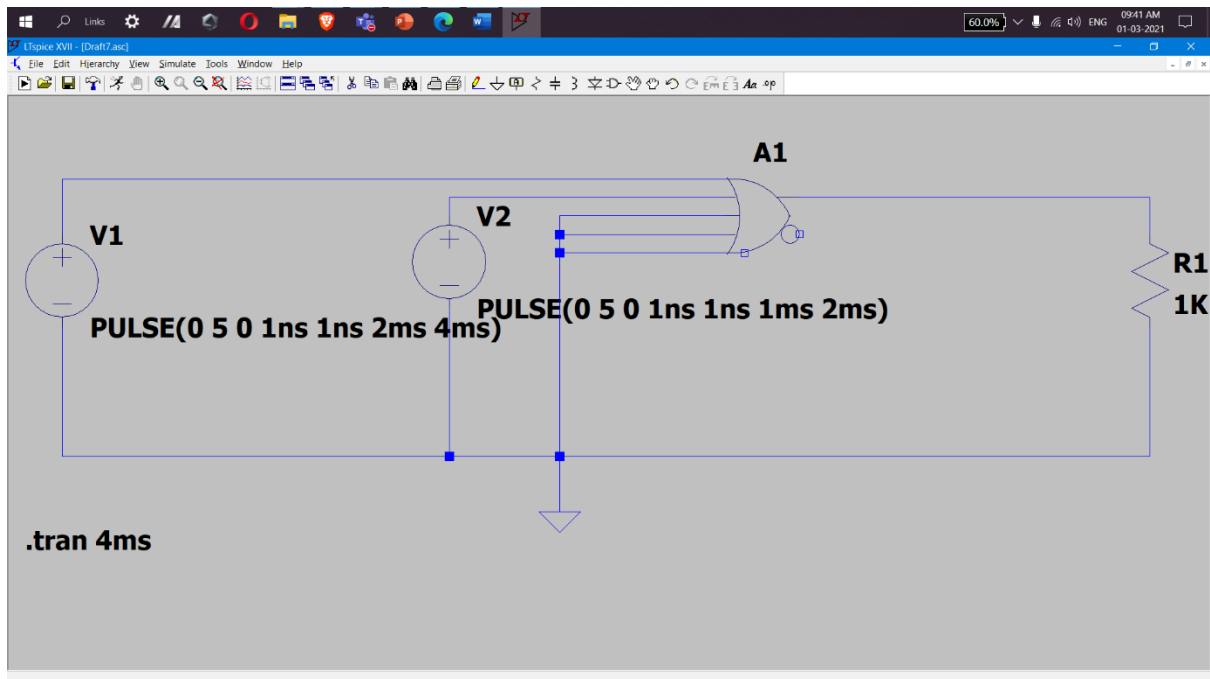


# OUTPUT

 


# NAND GATE

## DIAGRAM

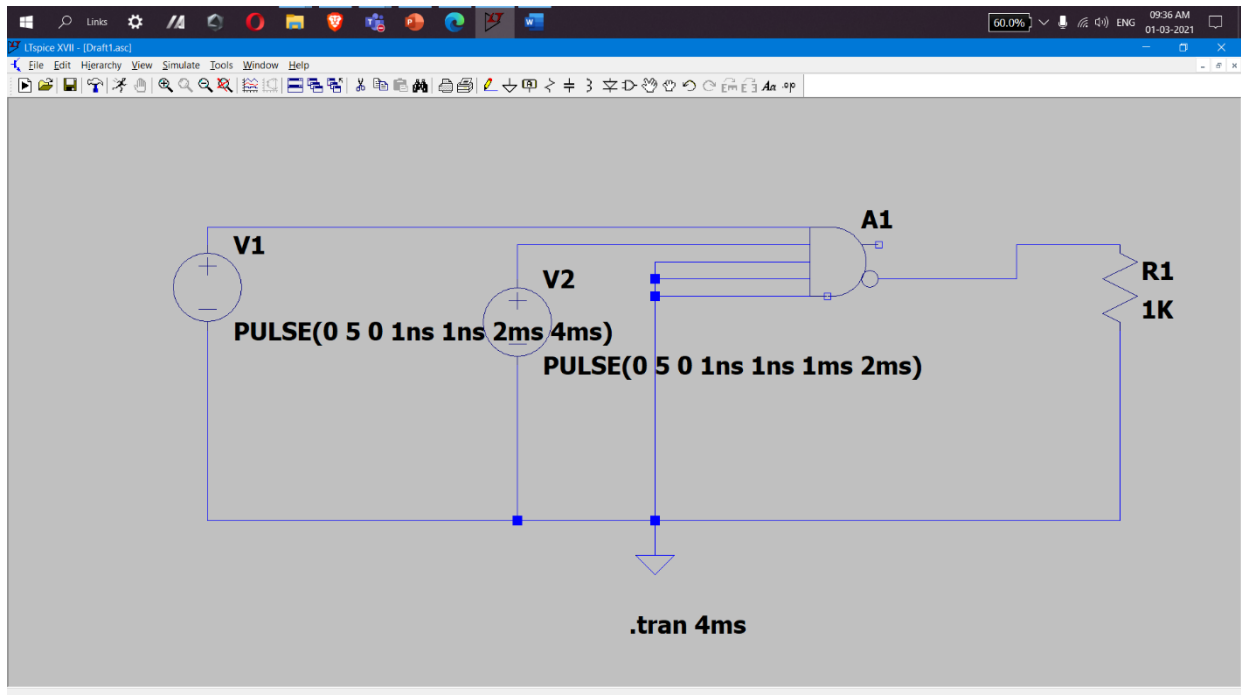


## OUTPUT

 


NOR GATE

DIAGRAM

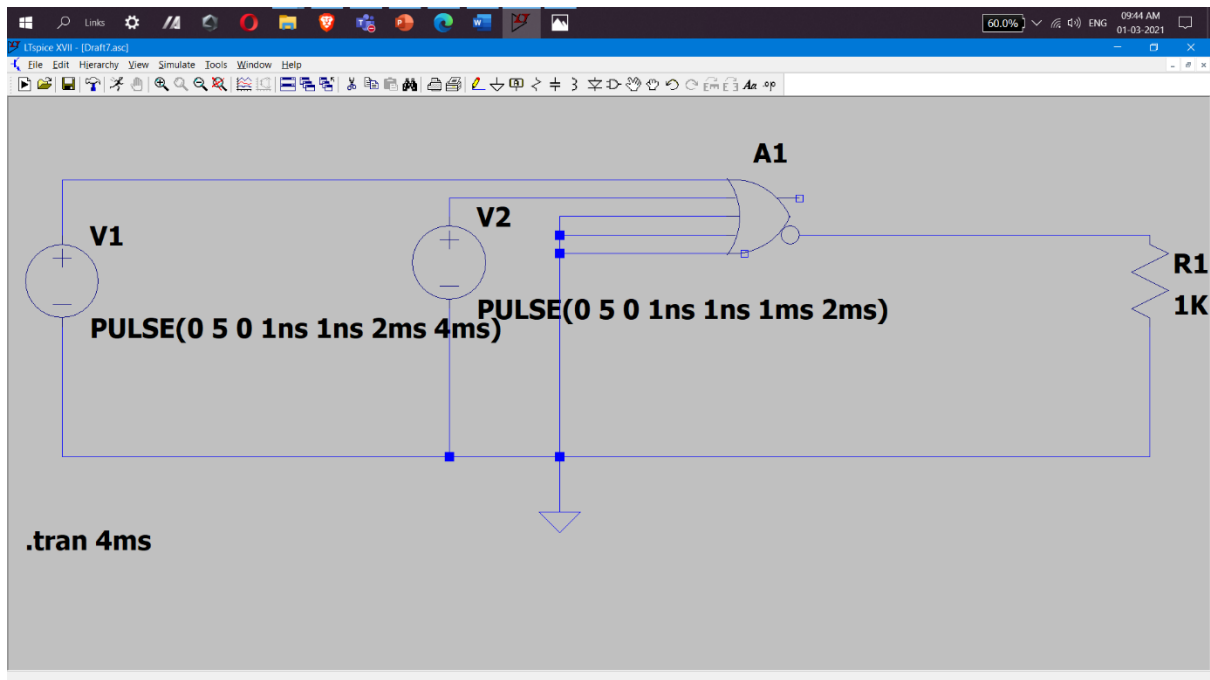


## OUTPUT

 

# XOR GATE

## DIAGRAM

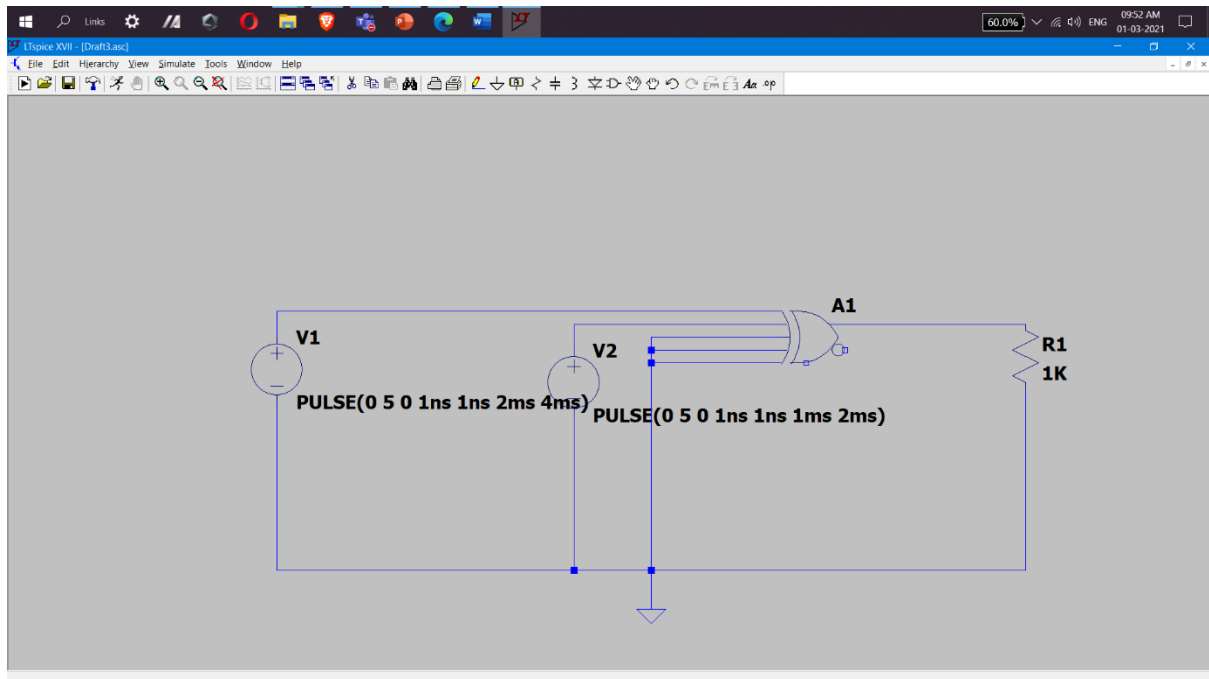

## OUTPUT



