## DLD LAB FAT

DATE-21-6-2021

BY
- ASHUTOSH ARDU
20BRS1262

a) Perform a conversion method strongly follows EX-OR gate operation between binary bits. They are used for error correction in digital Communication as well as to minimize correct in converting analog signal to digital signals?

AIM: To perform orner correction using X-ORgates.
[Using 7 bit Hamming (ade Correction method)
(Using Even provity Check)

- Open Lt spice
- Select the component wirbutten and search (xor), insert '9' xor gates for Hamming code correction
- Now, orgain go back to component section and search (voltage) and enter '7' voltages for checking 7 bits.
- Use the labels to get the outpett.
- In the end go to "Simulate" and tap "edit simulation (nd' and select "DCop pnit" and

click (ok).

- Now bare you have completed your circuit and now click on the run botton recieve the outpet.

Explaination:

7 bit Hamming (ade (even pravity))

D7 D6 D8 P4 D3 P2P1

Even parity of Pi=> Dz D5D7

Pi=> Dz D6D7


Pi=> D3D6D7

Pi=> D3D6D7

else Pr & Proutput " Pu Pr Pr
Hence, the bit out position (Pu Pir Pr)

needs to be corrected () 10


#### **CIRCUIT**

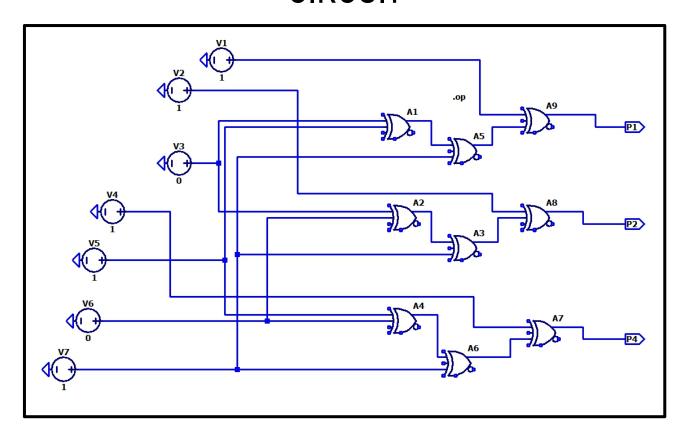


### **OUTPUT**

```
C:\Users\Ghost\OneDrive - vit.ac.in\Documents\LispiceXVII\rough.asc
       --- Operating Point ---
V(n003):
                0
                                voltage
V(n005):
                1
                                voltage
V(n004):
                1
                                voltage
V(n007):
                1
                                voltage
V(n006):
                                voltage
V(n001):
                1
                                voltage
V(n002):
                1
                                voltage
V(n010):
                 0
                                voltage
V(n009):
                0
                                voltage
V(n011):
                                voltage
V(n012):
                                voltage
V(n013):
                0
                                voltage
V(n008):
                                voltage
V(p4):
                1
                                voltage
V(p2):
                                voltage
V(p1):
                 1
                                voltage
I(V7):
                0
                                device_current
I(V6):
                 0
                                device_current
I(V5):
                                device_current
                0
I(V4):
                                device_current
I(V3):
                 0
                                device_current
I(V2):
                 0
                                device_current
I(V1):
                 0
                                device current
I8(A9):
                 -0
                                device_current
I7(A9):
                 0
                                device current
I8(A8):
                 -0
                                device_current
                 0
I7 (A8):
                                device_current
```
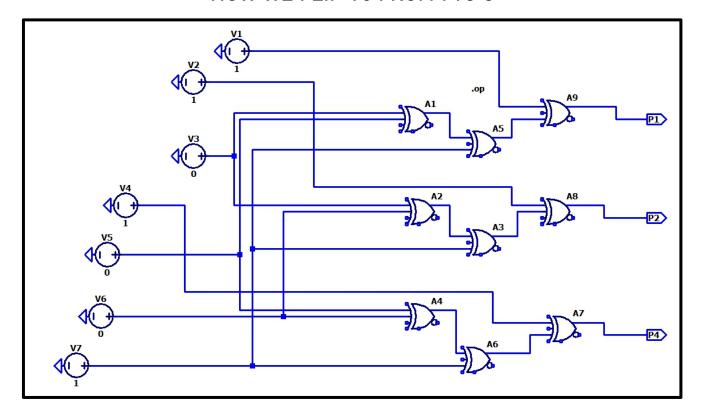
# AS YOU CAN SEE IN THE ABOVE PHOTO THE BIT AT POSITION 101 (P4.P2.P1) IS CORRUPTED. SO NOW WE CORRECT THAT BIT BY FLIPPING IT NOW WE FLIP V5 FROM 1 TO 0



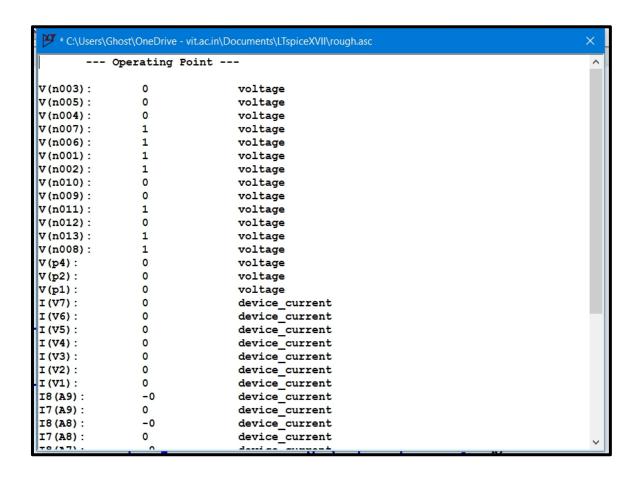NOW AS YOU CAN SEE AS WE FLIPPED V5 THE
HAMMING CODE IS NOW CORRECT, THAT IS THE REASON
WE GOT (P4, P2, P1) AS 000
MEANING NO BIT IS CORRUPTED



#### **RESULT AND INFERENCE**

AS FOR THE RECEIVED '11 0 11 0 1' AFTER ERROR CHECKING THE CIRCUIT THE BIT AT THE POSITION 1 0 1 (5) IS CORRUPTED.

SO V5 SHOULD FLIPPED TO 0 INSTEAD OF 1.